

# MultiWingSpan

Home Programming Web Design Computer Science Twisting Puzzles Arduino BBC micro:bit


## BBC micro:bit Shift Register (MicroPython)

### Introduction

The 74HC595 shift register is an integrated circuit that converts serial information to parallel. It requires 3 pins (as well as power) from the micro:bit but allows us to have a total of 8 outputs. This means that we can control 8 LEDs using only pins 0, 1 & 2.


This page describes how to use a shift register in MicroPython. The Python language, even cut down to this size, is way more flexible than any of the code editors. It is a nice thing to write the code for. Normally, you use built-in functions when doing this for other microcontrollers. This way, you do all of the digital logic yourself.

 The shift register used on this page looks like this and costs around 60p to buy, depending on the shop,


 
### The Circuit

Electronic components normally have a datasheet which explains how it works, what voltages it can tolerate and what each of the pins do. From the datasheet for this integrated circuit, the pinning diagram is as follows,



This looks a little complicated but can be understood if we take our time.

Pin	Connection	Description
VCC	3V	This provides power to the integrated circuit.
GND	GND	This is the connection to ground that completes our circuit.


### BBC Microbit

- + [Block Editor - The Basics](#)
- + [Block Editor - Components](#)
- + [Kodu - micro:bit Worlds](#)
- + [JavaScript Blocks](#)
- + [JavaScript Blocks - Exercises](#)
- + [Blocks - Bit:Bot](#)
- + [Blocks - Bit:Commander](#)
- + [MicroPython - Starting Off](#)
- + [MicroPython - Examples](#)
- [MicroPython - Components](#)
  - ★ [Introduction](#)
  - ★ [Buzzer With MicroPython](#)
  - ★ [LEDs With MicroPython](#)
  - ★ [Connecting micro:bits Together](#)
  - ★ [Extra Buttons](#)
  - ★ [Knock Sensor](#)
  - ★ [Rotary Encoder](#)
  - ★ [Potentiometer](#)
  - ★ [Soft Potentiometer](#)
  - ★ [Flex Sensor](#)
  - ★ [Tilt Sensor](#)
  - ★ [Reed Switch](#)
  - ★ [More Buttons](#)
  - ★ [Temperature Sensor](#)
  - ★ [7 Segment Display](#)
  - ★ [Reflectance Sensor](#)
  - ★ [Driving A Motor](#)
  - ★ [Shift Register](#)
  - ★ [Shifting In](#)
  - ★ [Neopixels](#)
  - ★ [IR Break Beam Sensor](#)
  - ★ [DIY MIDI Out](#)
  - ★ [PCF8574A Port Expander](#)
  - ★ [16x2 Character LCD Display](#)
  - ★ [SNES Controller](#)
- + [MicroPython - Breakout Boards](#)
- + [MicroPython - Exercises](#)
- + [MicroPython - Pi Accessories](#)
- + [MicroPython - Bit:Bot](#)
- + [MicroPython - Bit:Commander](#)
- + [MicroPython - Projects](#)
- + [MicroPython - Visual Basic](#)
- + [Other - Odds & Ends](#)



QA-QH	LEDs 1 - 8	These are the outputs. We connect them to the LEDs.
OE	GND	OE stands for output enable. The integrated circuit is enabled when we connect this to ground.
SRCLR	3V	We need to connect this pin to the power to enable the shift register.
SER	Pin 0	This is our <b>data</b> pin. We use this to send 1s and 0s to the shift register.
SRCLK	Pin 1	We call this the <b>clock</b> pin. We use this to tell the shift register to accept an input.
RCLK	Pin 2	We call this our <b>latch</b> pin. We use this to tell the shift register to output the mixture of high and low voltages we have previously sent.

 The notch on the integrated circuit tells you how to orient it when you put it into the breadboard. It goes at the top. Here is a diagram of the circuit you will need.



It looks complicated. It is easier to get the connections right if you follow the logic of the table above.

## Programming

In this program, the variable **value** stores the pattern of LEDs we want to light from our 8. Use this [Binary Counter](#) to see how counting from 0 to 255 produces a pattern of 1s and 0s on the 8 binary place values. The bits variable stores a list of these 1s and 0s, created with a nifty piece of Python. In the example, with a value of 255, all of the LEDs should come on. Try 170 to light alternate LEDs.

```
from microbit import *

pin0.write_digital(0)
pin1.write_digital(0)
pin2.write_digital(0)
value = 255
bits = [value >> i & 1 for i in range(7,-1,-1)]
for i in range(7,-1,-1):
    print(bits[i])
    pin0.write_digital(bits[i])
    pin1.write_digital(1)
    pin1.write_digital(0)
    pin2.write_digital(1)
    pin2.write_digital(0)
```

The for loop that goes from 7 to 0 is the important one. We write the 1 or 0 to pin0 (data) to set the value of each bit. Then we write a 1 and then a 0 to pin1 (clock). When the loop is done, we write a 1 and then a 0 to pin2 (latch) to make the shift register output the pattern.

Using a single number like this can make it quite easy to do some patterns with the LEDs. The following program uses a loop to light all of the LEDs, adding one at a time. The numbers used in the list are all 1 less than the binary place values. Think about the idea of place value and you can explain how and why this works.

```
from microbit import *

pin0.write_digital(0)
pin1.write_digital(0)
pin2.write_digital(0)
```

```
for value in [1,3,7,15,31,63,127,255]:
    bits = [value >> i & 1 for i in range(7,-1,-1)]
    for i in range(7,-1,-1):
        print(bits[i])
        pin0.write_digital(bits[i])
        pin1.write_digital(1)
        pin1.write_digital(0)
    pin2.write_digital(1)
    pin2.write_digital(0)
    sleep(100)
```

## Challenges

1. There has to be something interesting that you can do with so many LEDs. You could use them to show the amount of roll being sensed by the accelerometer, turning on different LEDs depending on whether the micro:bit is tilted to the left or right.
2. You could use some LEDs as a temperature indicator for a thermometer.
3. You could separate the LEDs into 2 groups of 4 and use them as a scoreboard for a digital game of rock, paper, scissors. After each round, the user should press button A or button B depending on which player won the round. When a player reaches 4, they win the game.
4. Pretty patterns can be made with this many LEDs. Look up a Larson Scanner. You can use the shift register to make one of these with your micro:bit.
5. 8 bits make a byte. Turn the LEDs into a binary counter that counts from 0 to 255. Use the buttons and you can allow the user to move up and down through the numbers from 0 to 255.
6. If you have an edge connector, swap pin0 for 8, 12 or 16. Then put a buzzer on pin0 and flash the lights along with notes from a tune or with each beat of a metronome you have made.